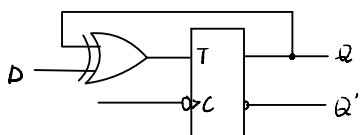


1. 如下图所示:



$$2.1) T_{clk} > T_{comb, max} + T_{clk2Q} + T_{setup} = 130ns$$

$$\Rightarrow f_{clk, max} \approx 7.69 \times 10^6 \text{ Hz}$$

2) $10\text{ns} + 3\text{ns} = 13\text{ns} < 15\text{ns}$

不能正常工作, 组合逻辑延时最小高 $15-10=5\text{ns}$.

3.

